

SR latch(function

- Circuit Diagram and Truth Table, functions of SR Latch:

ii. Active LOW input S-R Latch

 


Table Truth table for SR Flip Flop

S	R	Q	Q+
1	1	0	0
1	1	1	1
0	1	X	0
1	0	X	1
0	0	X	1

1. **Characteristic Function (Next State Function):**

$$Q_{\text{next}} = \bar{S} \cdot Q + S \cdot \bar{R} \cdot \bar{Q}$$

This equation expresses the next state of the latch (Q next) based on the current state (Q) and the inputs (S and R).

2. **Inverse Characteristic Function (Output Function):**

$$Q' = \bar{Q}$$

This equation expresses the inverse state of Q (Q') in terms of the normal state (Q).

- Verilog code:

```
module SR_Latch(
input S,R,
output Q, Qn
);

NAND nand1(.I1(~S), .I2(Qn), .O(Q));
NAND nand2(.I1(~R), .I2(Q), .O(Qn));

endmodule
```

- Testbench Code:

```
module SR_Latch_tb();
reg S,R;
wire Q,Qn;

SR_Latch srlatch1(S, R, Q,Qn);
initial
begin


S=0; R=0;
#10
S=0; R=1;
#10
```

```



S=1; R=0;
#10
S=0; R=0;
#10
S=0; R=1;
#10
S=0; R=1;
#10
$finish();
end
endmodule

```

Simulation Wave:

 

- RTL and Technology Schematics:

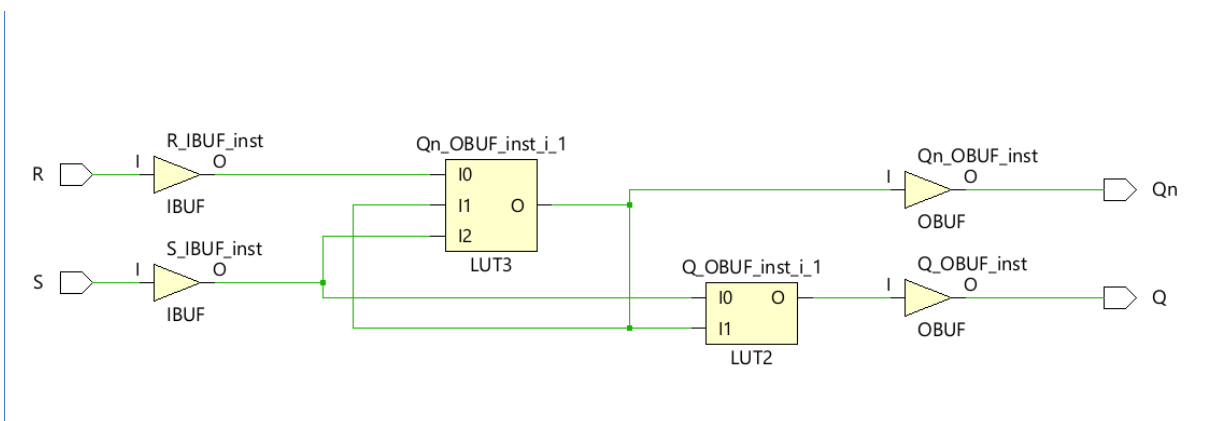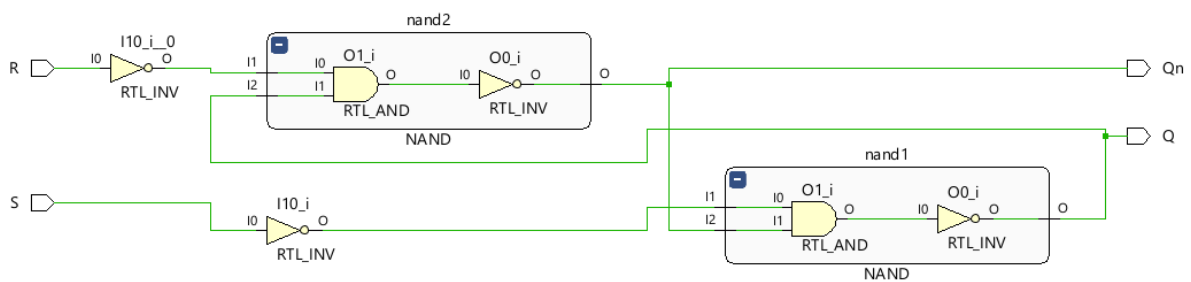


- Utilization and Timing Reports:

Maximum combinational delay is 10.159 and 2 LUTs used.


From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
<input checked="" type="checkbox"/> R	<input type="checkbox"/> Q	10.159	SLOW	3.465	FAST
<input checked="" type="checkbox"/> R	<input type="checkbox"/> Qn	9.620	SLOW	3.298	FAST
<input checked="" type="checkbox"/> S	<input type="checkbox"/> Q	9.739	SLOW	3.052	FAST
<input checked="" type="checkbox"/> S	<input type="checkbox"/> Qn	9.200	SLOW	3.115	FAST

Resource	Utilization	Available	Utilization %
LUT	2	63400	0.00
IO	4	210	1.90

 

D flipflop

- Circuit Diagram and Truth Table:

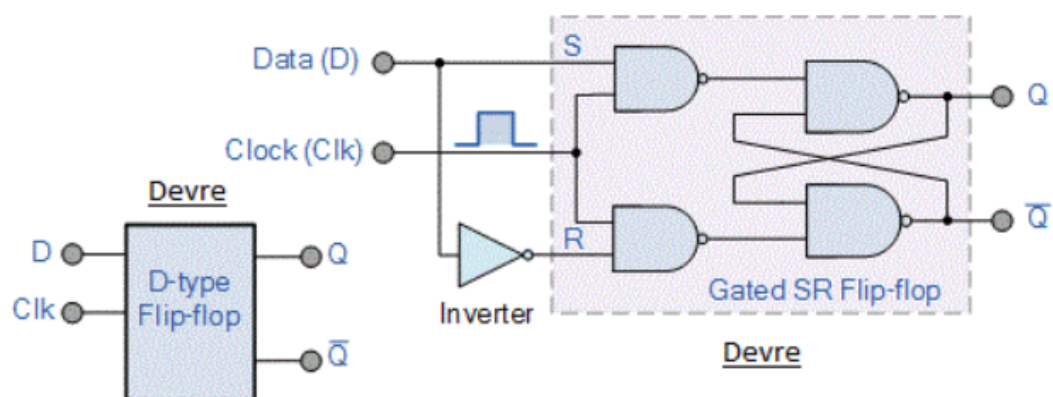

Input			Output	
D	reset	clock	Q	Q'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

- Verilog Code:

```

module D_FF (
    input CLK, D,
    output Q, Qn
);

wire setnot, resetnot, dnot;

NOT not1 (D,dnot);
NAND nand1 (D, CLK, setnot);
NAND nand2 (dnot, CLK, resetnot);
NAND nand3 (setnot, Qn, Q);
NAND nand4 (resetnot, Q, Qn);
endmodule

```

- Testbench Code:

```

module D_FF_tb;
reg CLK, D;
wire Q, Qn;
D_FF myD_FF (
    .CLK(CLK),
    .D(D),
    .Q(Q),
    .Qn(Qn)
);

initial begin
    CLK = 0;

```


```

    D = 0;
    #10 D = 1;
    #10 D = 0;
    #10 D = 1;
    #100 $finish;
end


always begin
    #5 CLK = ~CLK;
end
endmodule

```

- Simulation Wave:

 


- RTL and Technology Schematics:

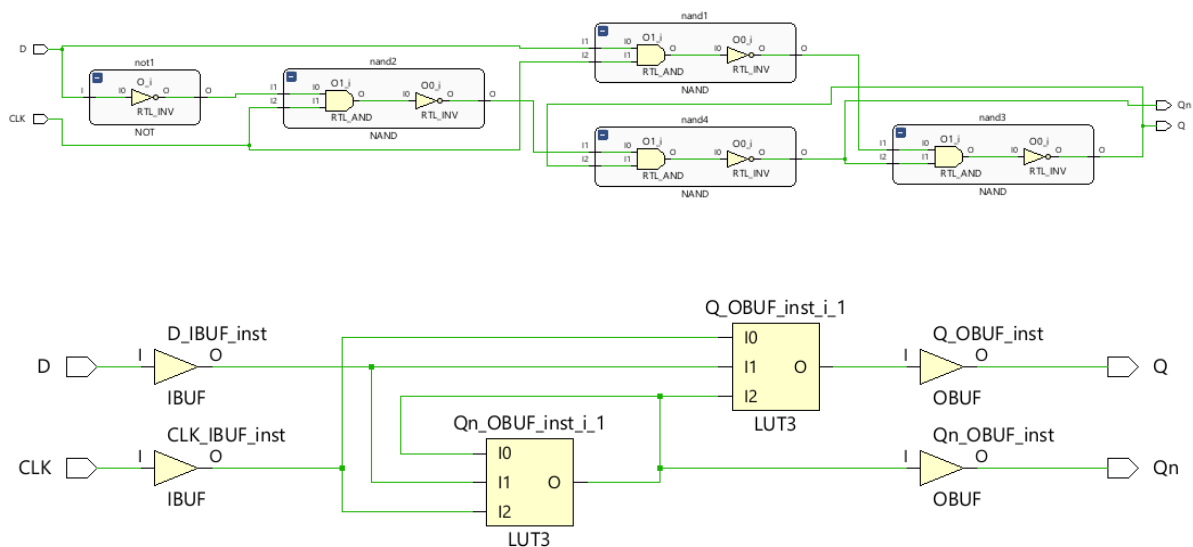

- Utilization and Timing Reports:

2 LUTs used and maximum combinational delay is 9.357ns. A period longer than this value is required. Hence, the clock's maximum frequency is limited to 0.107 GHz. This ensures that the design is capable of completing the longest path within a single period.

Resource	Utilization	Available	Utilization %
LUT	2	63400	0.00
IO	4	210	1.90

 

From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
<input checked="" type="checkbox"/> CLK	<input checked="" type="checkbox"/> Q	9.357	SLOW	2.647	FAST
<input checked="" type="checkbox"/> CLK	<input checked="" type="checkbox"/> Qn	8.418	SLOW	2.525	FAST
<input checked="" type="checkbox"/> D	<input checked="" type="checkbox"/> Q	8.846	SLOW	2.415	FAST
<input checked="" type="checkbox"/> D	<input checked="" type="checkbox"/> Qn	7.907	SLOW	2.282	FAST

D flipflop master slave

- Verilog Code:

```

module Master_Slave_D_FF(
    input D,CLK,
    output Q, Qn
);

    wire Qm, Qmnot;

    D_FF master(CLK, D, Qm, Qmnot);
    D_FF slave(!CLK, Qm, Q, Qn);

endmodule

```

- Testbench Code:

```

module Master_Slave_D_FF_tb;
    reg D, CLK;
    wire Q, Qn;

```

```

Master_Slave_D_FF myD_FF (
    .D(D),
    .CLK(CLK),
    .Q(Q),
    .Qn(Qn)
);


initial begin
    D = 0;
    CLK = 0;
    #5 D = 1;
    #5 CLK = 1;
    #5 CLK = 0;
    #5 D = 0;
    #22 D=1;
    #100 $finish;
end

always begin
    #2 CLK = ~CLK;
end


endmodule



```

- Simulation Wave:

 

- RTL and Technology Schematics:

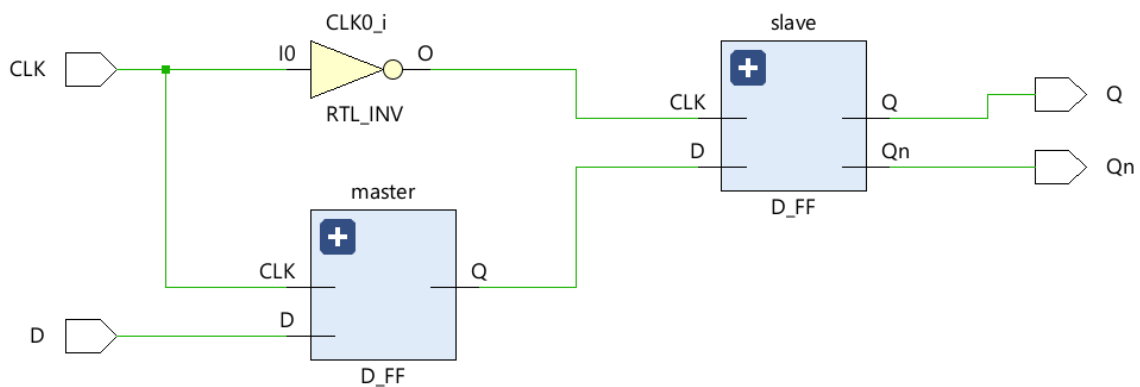

  


- Timing and Utilization Reports:

Maximum combinational delay is 9.474 and 3 LUTs are used.

From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
✓ CLK	✓ Q	9.474	SLOW	2.728	FAST
✓ CLK	✓ Qn	8.840	SLOW	2.680	FAST
✓ D	✓ Q	8.856	SLOW	2.605	FAST
✓ D	✓ Qn	8.222	SLOW	2.415	FAST

Resource	Utilization	Available	Utilization %
LUT	3	63400	0.00
IO	4	210	1.90

 

- The Master-Slave D Flip-Flop is a digital circuit element composed of two stages. The first stage (master) performs the data sampling process, while the second stage (slave) transfers this data to the output. The master stage responds to the rising or falling edge of the clock signal, whereas the slave stage responds to the opposite

edge. This two-stage process mitigates potential issues observed in single-stage flip-flops. The clock signal ensures synchronized operation, preventing problems like metastability. In summary, the Master-Slave D Flip-Flop is utilized to store and transfer data in a controlled manner. In our Flip-Flop the falling edge of the clock effects the output.



Fig.4: Time diagram for Master-Slave Flip-Flop.

D flipflop Behavioral

- Verilog Code:

```
module D_FF_behav (
    input CLK, D,
    output Q, Qn
);

wire setnot, resetnot, dnot;
reg ff;

always@ (posedge CLK) begin
    ff <= D;
end

assign Q = ff;
assign Qn = !ff;

endmodule
```

- Testbench Code:

```
module D_FF_behav_tb;

reg CLK, D;
wire Q, Qn;

D_FF_behav myD_FF_behav (
    .CLK(CLK),
    .D(D),
    .Q(Q),
```

```

        .Qn(Qn)
    );

initial begin
    CLK = 0;
    D = 0;


    #5 D = 1;
    #5 CLK = 1;
    #5 CLK = 0;
    #5 D = 0;
    #43 D=1;
    #100 $finish;
end

always begin
    #2 CLK = ~CLK;
end


endmodule


```

- Simulation Wave

 


- RTL and Technology Schematics

 

 

- Utilization Report:

Resource	Utilization	Available	Utilization %
LUT	1	63400	0.00
FF	1	126800	0.00
IO	4	210	1.90

 

8bit Register

- Verilog Code:

```

module bit8_reg(
    input [7:0] IN,
    input CLK,
    input CLR,
    output reg [7:0] OUT
);

always @(posedge CLK or posedge CLR) begin
    if (CLR==1'b1)
        OUT = 8'b0000_0000;
    else OUT=IN;
end
endmodule

```

- Testbench Code:

```

module tb_bit8_reg;

```

```

reg [7:0] IN;
reg CLK, CLR;
wire [7:0] OUT;
bit8_reg myBit8Reg (
    .IN(IN),
    .CLK(CLK),
    .CLR(CLR),
    .OUT(OUT)
);

initial begin
    IN = 8'b10101010;
    CLK = 0;
    CLR = 0;


    #5 CLR = 1;
    #5 CLR = 0;
    #10 IN = 8'b11001100;
    #5 CLK = 1;
    #5 CLK = 0;
    #100 $finish;
end

always begin
    #5 CLK = ~CLK;
end



endmodule

```

- Simulation Wave:arada bi tane daha clr

 


- RTL and Technology Schematics:

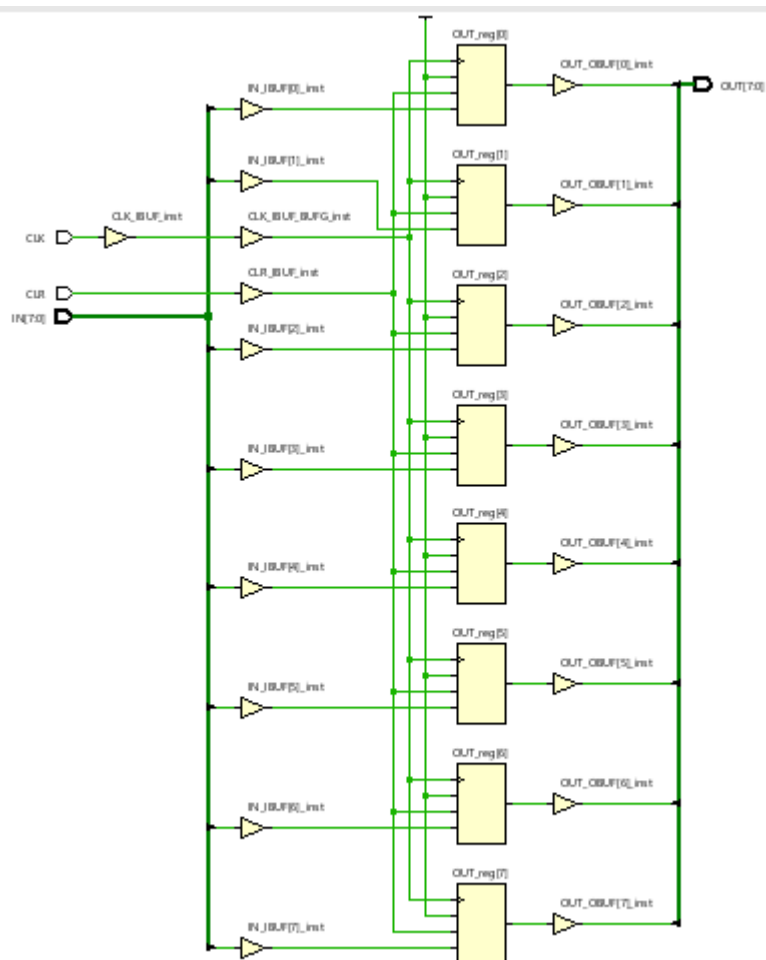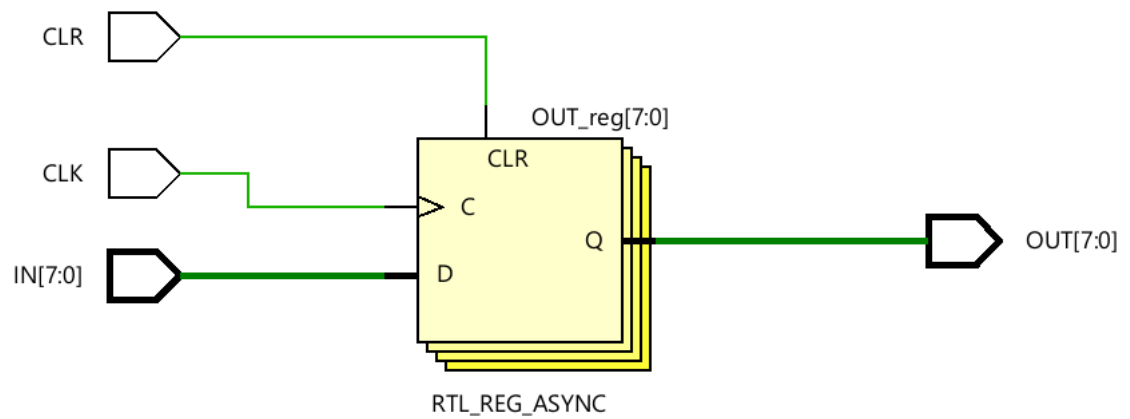


- Utilization Reports:
8 LUTs are used.

Resource	Utilization	Available	Utilization %
FF	8	126800	0.01
IO	18	210	8.57

 

We can define 4x8 bit of register array by: `reg [7:0] myArray [0:3];`

BRAM

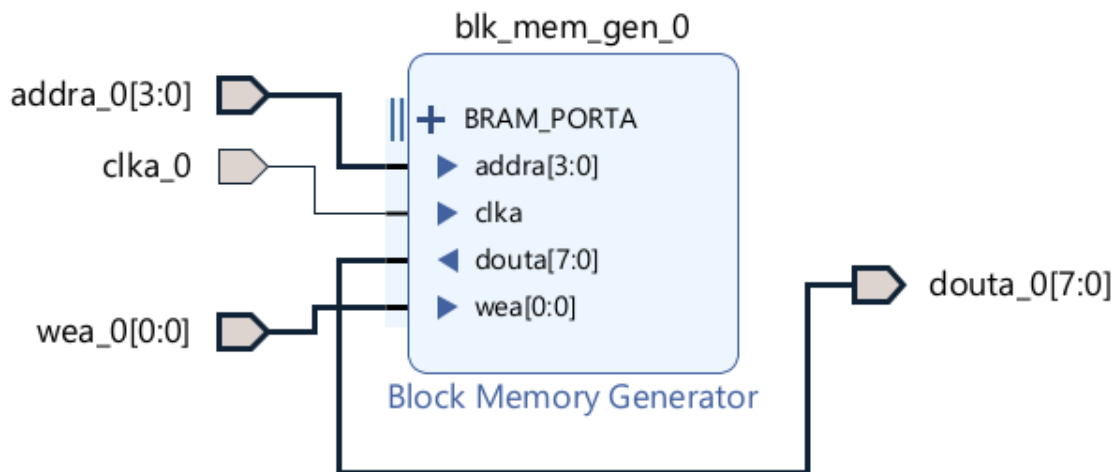

- Verilog Code:

```

module Top_BRAM(
    input CLK, WE,

```

```

    input [3:0] addr,
    output [7:0] dout

);
    wire [7:0] din;

    BRAM brami (.clka_0(CLK), .wea_0(WE), .addra_0(addr),
    .douta_0(dout));
endmodule

```

- **Testbench Code:**

```

module top_bram_TB( );
wire [7:0] DOUT;
reg [7:0] DIN;
reg [3:0] ADDR;
reg CLK;
reg WE=0;

integer count=0;
Top_BRAM uut(CLK, WE, ADDR, DOUT);
initial
begin
CLK=0;
forever #5 CLK=~CLK;
end
initial
begin
while (count<8)
begin
ADDR=count;
#20 count=count+1;
end
#20
$finish;
end
endmodule

```



- My memory.coe file:

```
MEMORY_INITIALIZATION_RADIX=2;
MEMORY_INITIALIZATION_VECTOR=
00000100,
00000000,
00000010,
00000000,
00000000,
00000010,
00000000,
00000000,
00000011,
00000100,
00000000,
00000010,
00000000,
00000000,
00000010,
00000000,
00000000,
00000010,
00000000,
00000011;
```

- Simulation results:




- RTL and Technology Schematics:

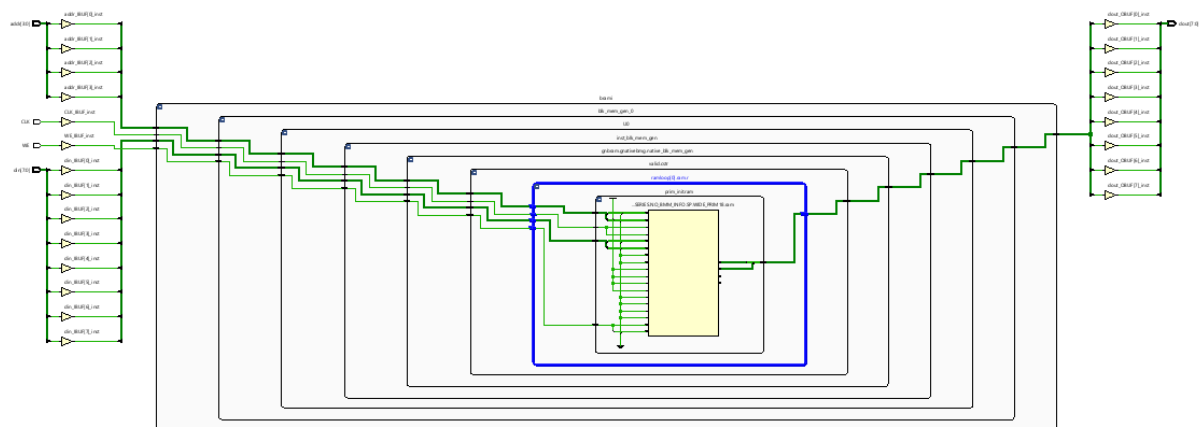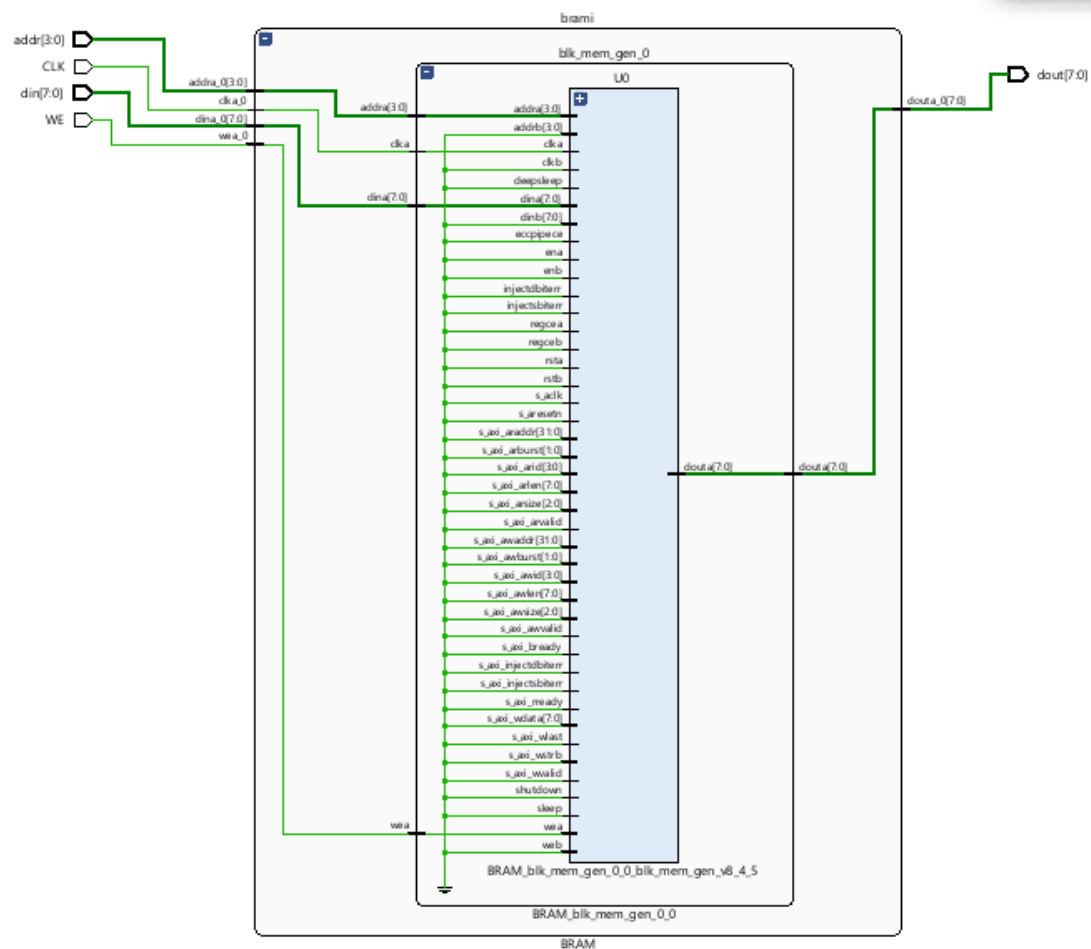

Utilization report:

Resource	Utilization	Available	Utilization %
BRAM	0.50	135	0.37
IO	22	210	10.48

 

- The ``address`` port specifies the address to access in the memory cell. The ``clk`` port represents the clock signal that synchronizes memory operations. The ``we`` port controls whether a write operation will occur. The ``dout`` port reads the data from the memory cell at the specified address. Such a structure is commonly used for applications like program memory or data memory, with memory access and control forming the core of the design.