

Digital System Design Applications

PROJECT - 2

SEQUENTIAL CIRCUITS

EHB436E
CRN: 10345

Group:1

Nurgül Gürler
040190251


Hatice Nur Andı
040200203

Design Steps

1. State Diagram

The circuit purpose is detection of the two 4 bit numbers separately. In our case, the chosen school number is 040200203. So, A=0000 and B=0011.

Here is the state diagram of our design;

 

In our design, the circuit detects both A and B and when one of these occurs, two counter is counting it. So, when second one occurs for A and B separately, the circuits goes to another state that indicated as S which is denotes the lock state.

Here is the code for state machine;

```
`timescale 1ns / 1ps

module state_machine(
  input X,
  input CLK,
  input RST,
  output Y
);
```

```
reg [3:0] state;
reg [1:0] counterA=2'b00, counterB=2'b00;
reg flaga=0, flagb=0;
parameter

A= 4'b0000,
B= 4'b0001,
C= 4'b0011,
D= 4'b0010,
E= 4'b0110,
F= 4'b0111,
G= 4'b0101,
S= 4'b1111;

always @(posedge RST or posedge CLK)

begin

if (RST) begin
    state<=A;
    counterA<=0;
    counterB<=0;
end

else begin

case (state)

    A: if (X) state <=A;
       else state <=B;

    B: if (X) state <=A;
       else state <=C;

    C: if (X) state <=F;
       else state <=D;

    D: if (X) state <=F;
       else begin
           state <=E;
       end

    E: begin
        if (counterA < 2'b10) counterA <= counterA+1;
        if (counterA==2'b01) begin
            if (X==0)begin
```

```
        state <=S;
    end
end
    else begin
        state <=F;
    end

end

F: begin
    if (counterB==2'b01) begin
        if (X==1) state<=S;
        else state<=B;
    end

    else if(X) state <=G;
    else begin state <=B;
    end
end

G: begin
    if (counterB < 2'b10) counterB<= counterB+1;
    if (X) state <=A;
else begin
state <=B;
end
end

S: state <=S;

default state <= A ;


endcase

    if (counterB==2'b10 || counterA==2'b10) begin
        state<=S;
    end
end
end

assign Y = (state==S) | (state==E) | (state==G);

endmodule
```

2. Encoding the states

 

To implement the circuit with less power consumption, we coded the states systematically as changing only one bit when state changes according to the relation of the states.

3. FSM Reduction Techniques


State Elimination, Equivalent State Identification, State Encoding, Dead State Elimination, State Assignment, Partitioning, Sequential Equivalence Checking, Optimizing Transitions, and Technology Mapping are reduction techniques used in finite state machines.

One of the FSM reduction technique is the equivalent state reduction. For this technique, the equivalent states in terms of state transition, output and input are eliminated to one state. In our state machine, we consider this method from start so, our machine has not got any states that needs to be reduced.

4. Post Implementation Reports

From the post-implementation reports, here is the some report results;

Resource	Utilization	Available	Utilization %
LUT	10	63400	0.02
FF	7	126800	0.01
IO	4	210	1.90

 

The total LUT count is 10, FF count is 7 and lastly, total IO port number is 4 according to the utilization report.

From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
FSM_sequential_state_reg[0]/C	Y	6.902	4.100	2.802	∞	
X	FSM_sequential_state_reg[1]/D	4.101	1.733	2.368	∞	input port clock
X	FSM_sequential_state_reg[2]/D	3.961	1.733	2.228	∞	input port clock
X	FSM_sequential_state_reg[0]/D	3.861	1.733	2.127	∞	input port clock
RST	FSM_sequential_state_reg[2]/CLR	2.538	1.478	1.060	∞	input port clock
RST	counterA_reg[0]/CLR	2.538	1.478	1.060	∞	input port clock
RST	counterA_reg[1]/CLR	2.538	1.478	1.060	∞	input port clock
RST	FSM_sequential_state_reg[0]/CLR	2.533	1.478	1.056	∞	input port clock
RST	counterB_reg[0]/CLR	2.533	1.478	1.056	∞	input port clock
RST	counterB_reg[1]/CLR	2.533	1.478	1.056	∞	input port clock

On the view of timing, the maximum path delay is 6.902 ns. So, the maximum frequency of the circuit is 144.8 MHz.

5. Constraints

“set_max_delay -from [get_cells -hierarchical *] -through [get_nets -hierarchical *] -to [get_cells -hierarchical *] 1.000”

The design could not achieve the goal.

From	To	Total Delay	Logic Delay	Net Delay	Requirement
FSM_sequential_state_reg[1]/C	FSM_sequential_state_reg[0]/D	2.488	0.704	1.784	3.0
FSM_sequential_state_reg[1]/C	FSM_sequential_state_reg[1]/D	2.404	0.704	1.700	3.0
counterA_reg[1]/C	FSM_sequential_state_reg[2]/D	2.282	0.839	1.443	3.0
FSM_sequential_state_reg[0]/C	counterA_reg[0]/D	1.482	0.580	0.902	3.0
FSM_sequential_state_reg[0]/C	counterA_reg[1]/D	1.508	0.606	0.902	3.0
counterB_reg[1]/C	counterB_reg[0]/D	1.415	0.715	0.700	3.0
counterB_reg[1]/C	counterB_reg[1]/D	1.443	0.743	0.700	3.0

6. Waveforms

Here is the testbench code;

```
`timescale 1ns / 1ps

module TB();
    reg clk,x;
    reg [41:0] in;
    wire z;
```

```
reg reset;

state_machine uut(.X(x), .CLK(clk), .Y(z), .RST(reset));

integer i;
initial begin
reset=1'b0;
clk=1'b0;
in=42'b00100100000110110000111100000111100000011;
i=41;
while(i>=0)
begin


if (i==1) begin
reset<=1;
#2
reset<=0;
end

clk<=~clk;
#2
x=in[i];
#5
clk<=~clk;
i=i-1;
#5;

end
$finish;

end
endmodule
```

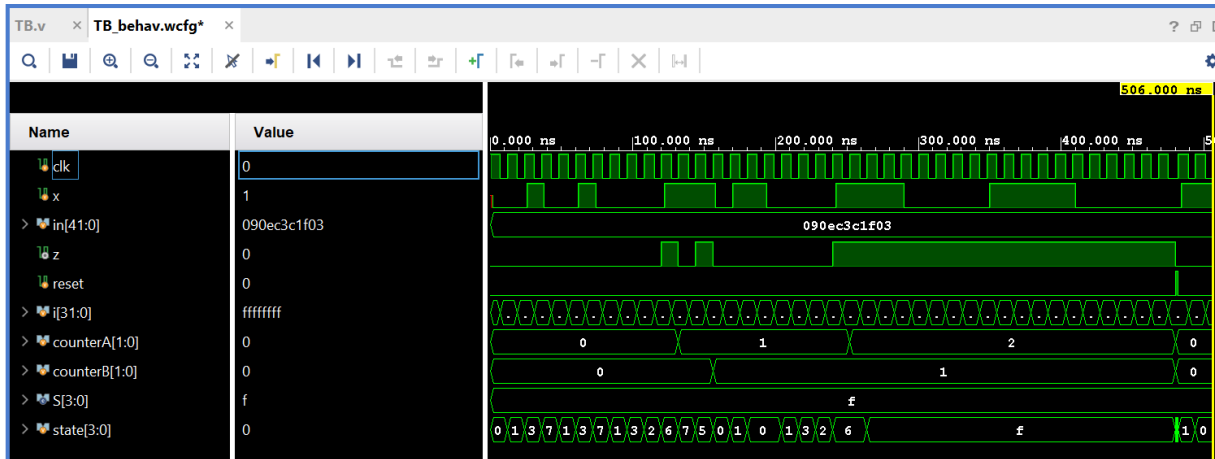For this code, the related waveform is attached below. We can see the detection of first A and B and the second A with the lock state. At the end, we can see the RST signal and escaping from the lock state.




Here is another example;

```

integer i;
initial begin
    reset=1'b0;
    clk=1'b0;
    in=42'b001001000011101100111111000001111100000011;
    i=41;
    while (i>=0)
    begin

```

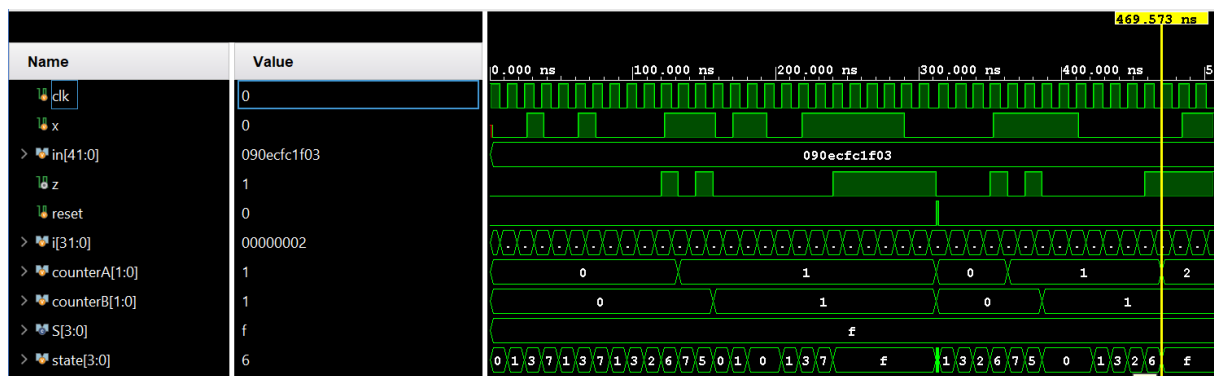In this input X, we are testing the circuit abilities that are detecting A and B when overlap situation, Lock state when the second B comes. Also we added a reset signal after lock state to see escaping from lock state.



In this waveform, we can see that after A and B detected once, when the second B came, the circuit can go to the lock state until RST signal come. After reset occur, the circuit can escape the lock state.

7. Circuit Type

Our circuit is a Moore Type circuit, the output is only depends on the state changes, not also inputs. There are no faulty outputs also.